






MEDIDOR DE INDUCTORES







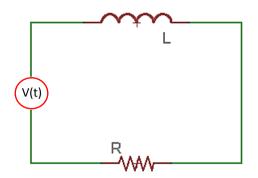Primera aproximación considerando un inductor ideal:



$$V_L(t) = L \frac{di}{dt}$$

$$\begin{cases} L i'(t) + R i(t) = V(t) \\ i(0) = 0 \end{cases}$$


$$i(t) = \frac{V}{R} - \frac{V e^{-\frac{R}{L}t}}{R} = \frac{V}{R} \left(1 - e^{-\frac{R}{L}t}\right)$$
[1]

Damos valores aleatorios a los componentes a fin de ver la curva resultante:

R = 10 Ohm

V = 5 v

L = 0.1 Hy

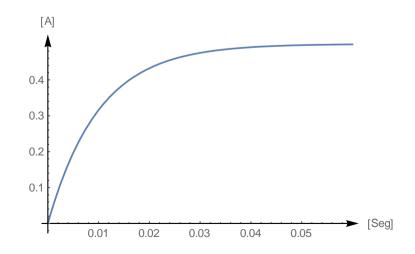





$$\tau = \frac{L}{R} \ [Seg]$$

Reemplazamos τ en [1]:

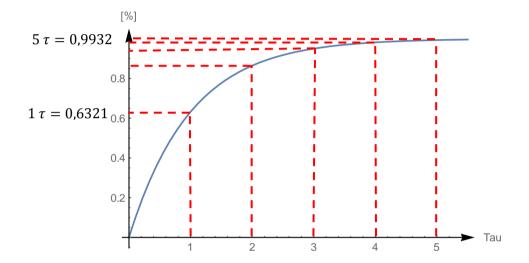
$$i(t) = 1 - \frac{1}{e^{\frac{t}{\tau}}}$$



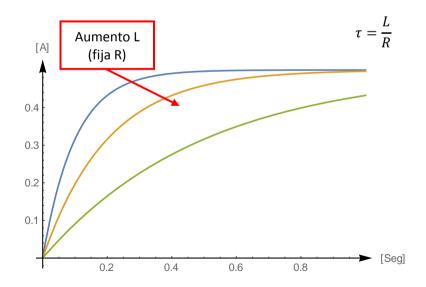Analizamos la familia de curvas en función del valor de τ :





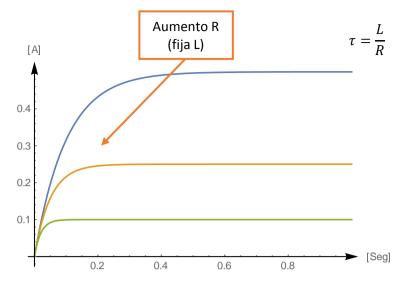

Multiplicamos m. a m. a [1] por "R":

$$\underbrace{R \ i(t)}_{V_R(t)} = R \ \frac{V}{R} \left(1 - e^{-\frac{R}{L}t} \right)$$

$$V_R(t) = V\left(1 - e^{-\frac{R}{L}t}\right)$$

$$\frac{V_R}{V} = 1 - e^{-\frac{R}{L}t}$$

$$\frac{V_R}{V} - 1 = -e^{-\frac{R}{L}t}$$

$$1 - \frac{V_R}{V} = e^{-\frac{R}{L}t}$$

$$\ln\left(1 - \frac{V_R}{V}\right) = \ln\left(e^{-\frac{R}{L}t}\right)$$

$$\ln\left(1 - \frac{V_R}{V}\right) = \left(-\frac{R}{L} t\right) \underbrace{\ln(e^1)}_{=1}$$






$$-\frac{\ln\left(1-\frac{V_R}{V}\right)}{R\ t} = \frac{1}{L}$$

$$L = -\frac{R t}{\ln\left(1 - \frac{V_R}{V}\right)}$$

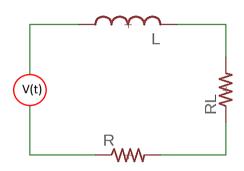Segunda aproximación considerando la R interna del inductor:



$$\begin{cases} L i'(t) + R i(t) + R_L i(t) = V(t) \\ i(0) = 0 \end{cases}$$

$$i(t) = -\frac{V(t)\left(-1 + e^{\frac{(-R - R_L)}{L}t}\right)}{R + R_L} [2]$$

$$\underbrace{R\,i(t)}_{V_R(t)} = -\frac{V\,\left(-1 + e^{\frac{\left(-R - R_L\right)}{L}\,t}\right)}{R + R_L}\,R$$

$$-\frac{V_R\left(R+R_L\right)}{V\,R} = -1 + e^{\frac{\left(-R-R_L\right)}{L}t}$$

$$1 - \frac{V_R (R + R_L)}{V R} = e^{\frac{(-R - R_L)}{L}t}$$





$$\ln\left(1 - \frac{V_R (R + R_L)}{V R}\right) = \ln\left(e^{\frac{(-R - R_L)}{L}t}\right)$$

$$\ln\left(1 - \frac{V_R (R + R_L)}{V R}\right) = \frac{(-R - R_L)}{L} t \ln(e^1)$$

$$L = -\frac{(R + R_L) t}{\ln\left(1 - \frac{V_R (R + R_L)}{V R}\right)}$$